

FPGA LPM Component

Stop-Watch Counter


JAICHANGPARK

20181017


Aim

- Use the FPGA to create a stopwatch counter.
- Use the internal clock of the DE2 board to create a frequency divider counter and check the result.
- Create a counter that increments every second..


➤ Create new File

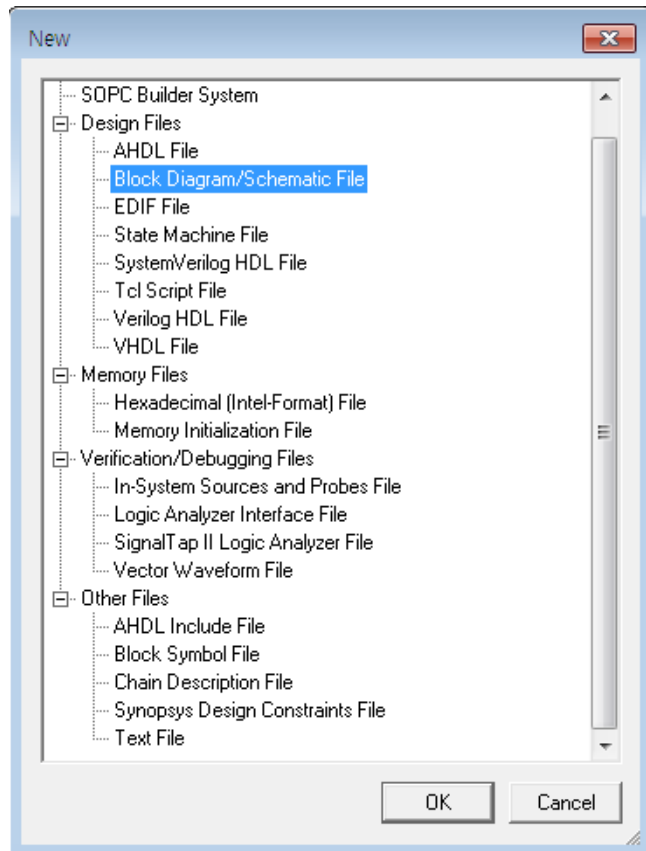

➤ Choose new Symbol block


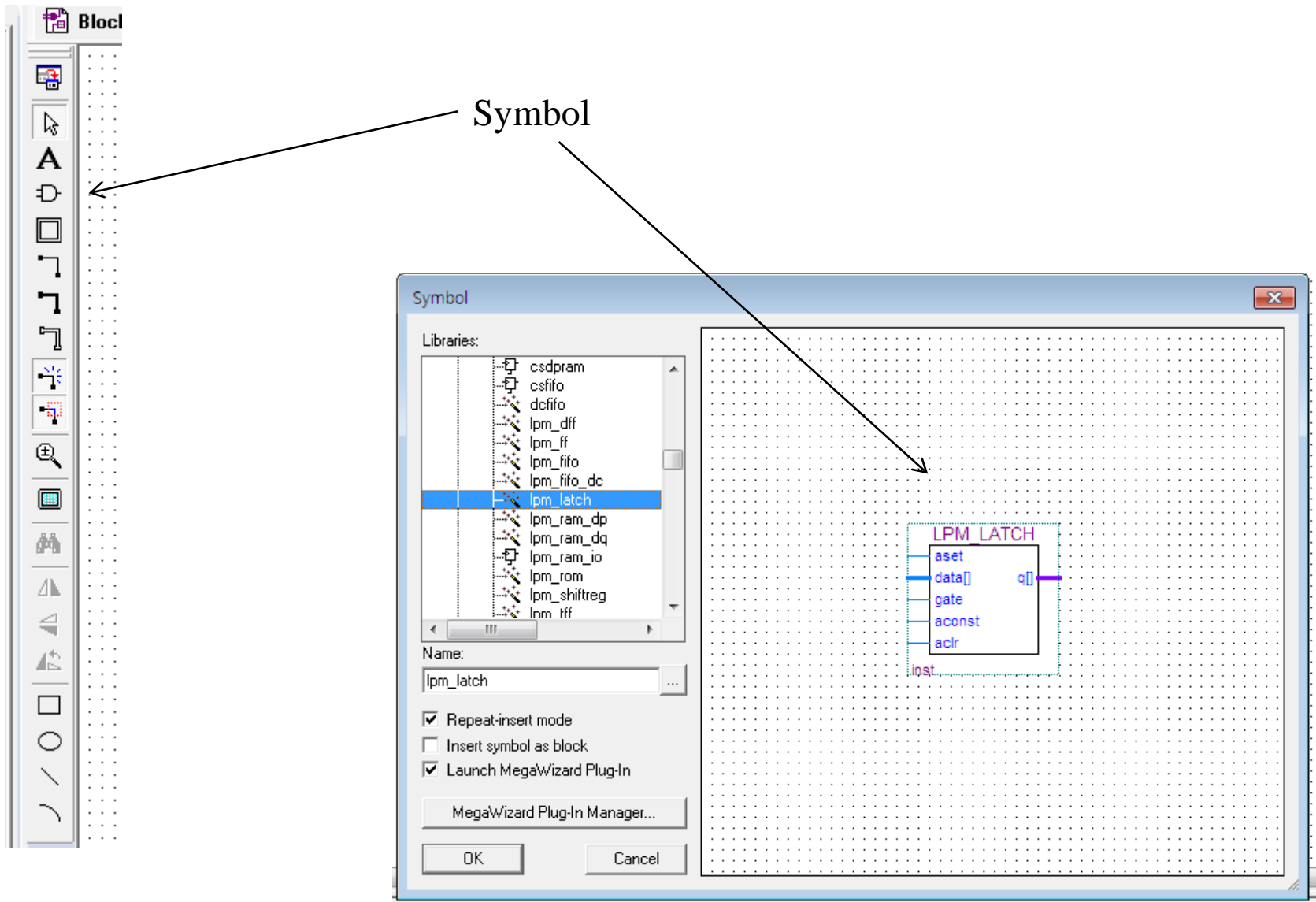


➤ Mega Wizard plug- in manager

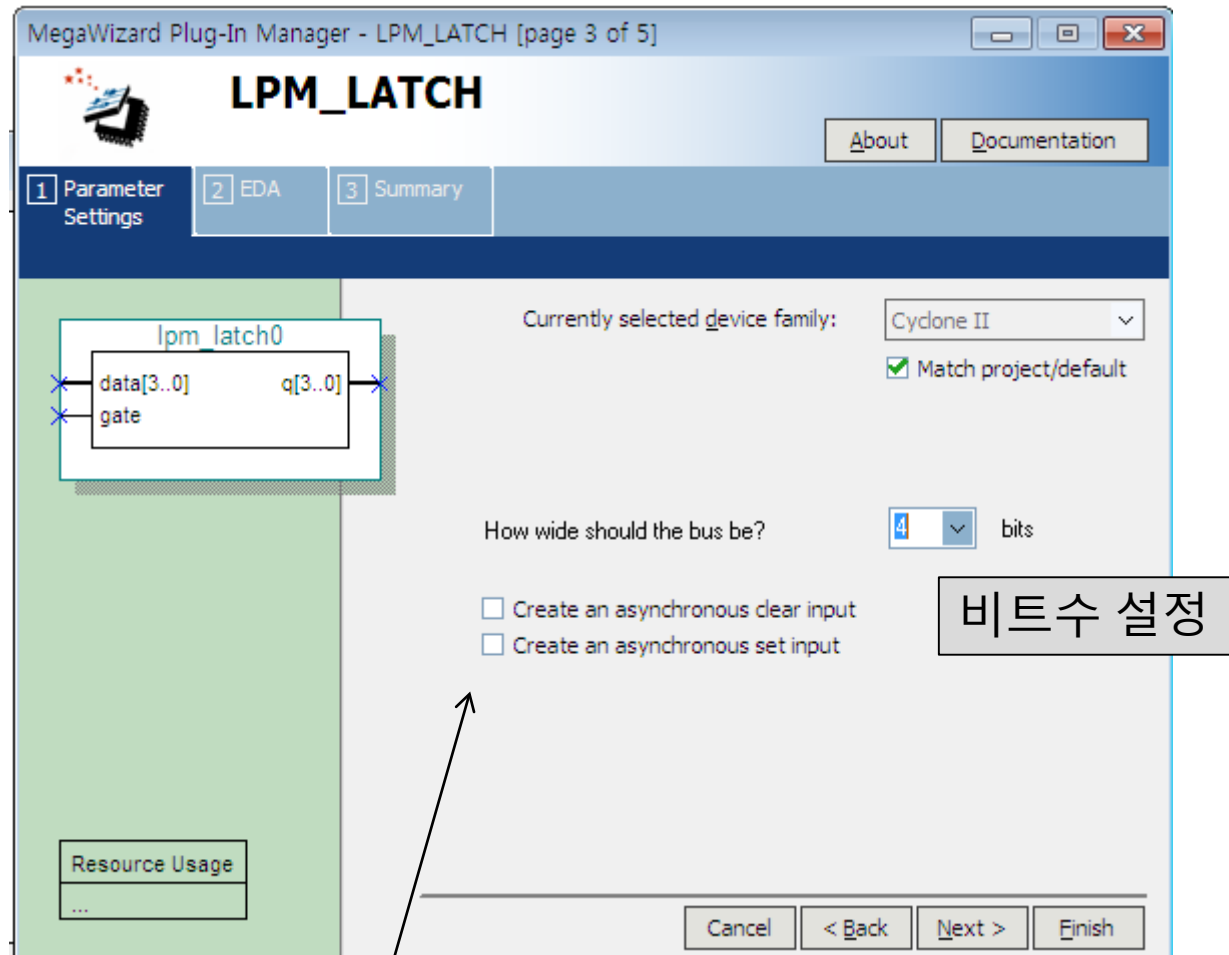

Check none


➤ 배치 영역 설정

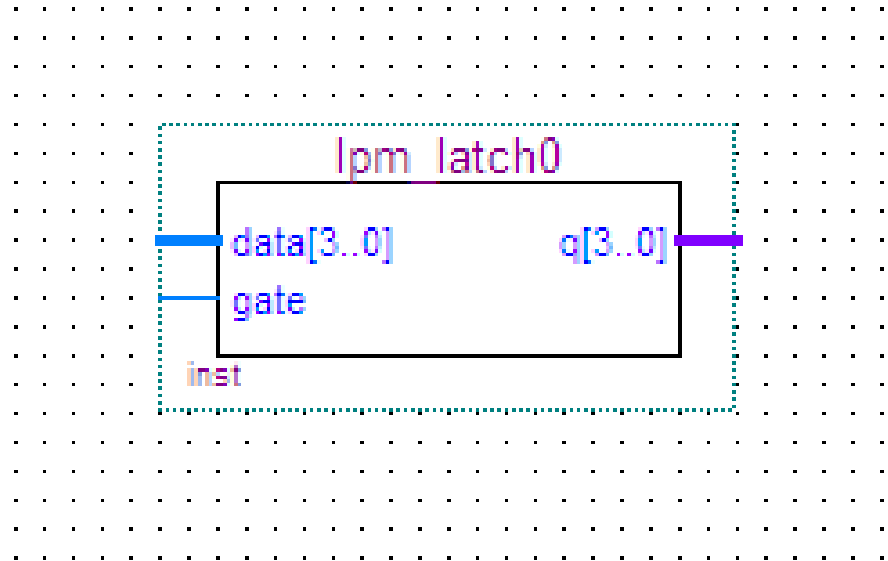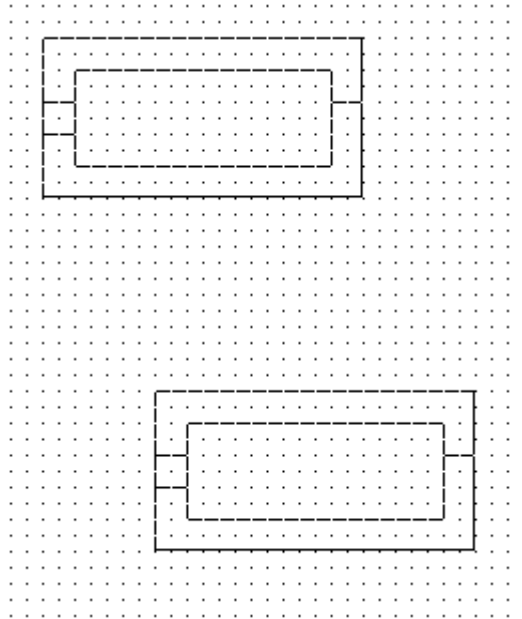

Place the set lpm block on the sketch.

First of all, I created a try block by practice and put it on my sketch.

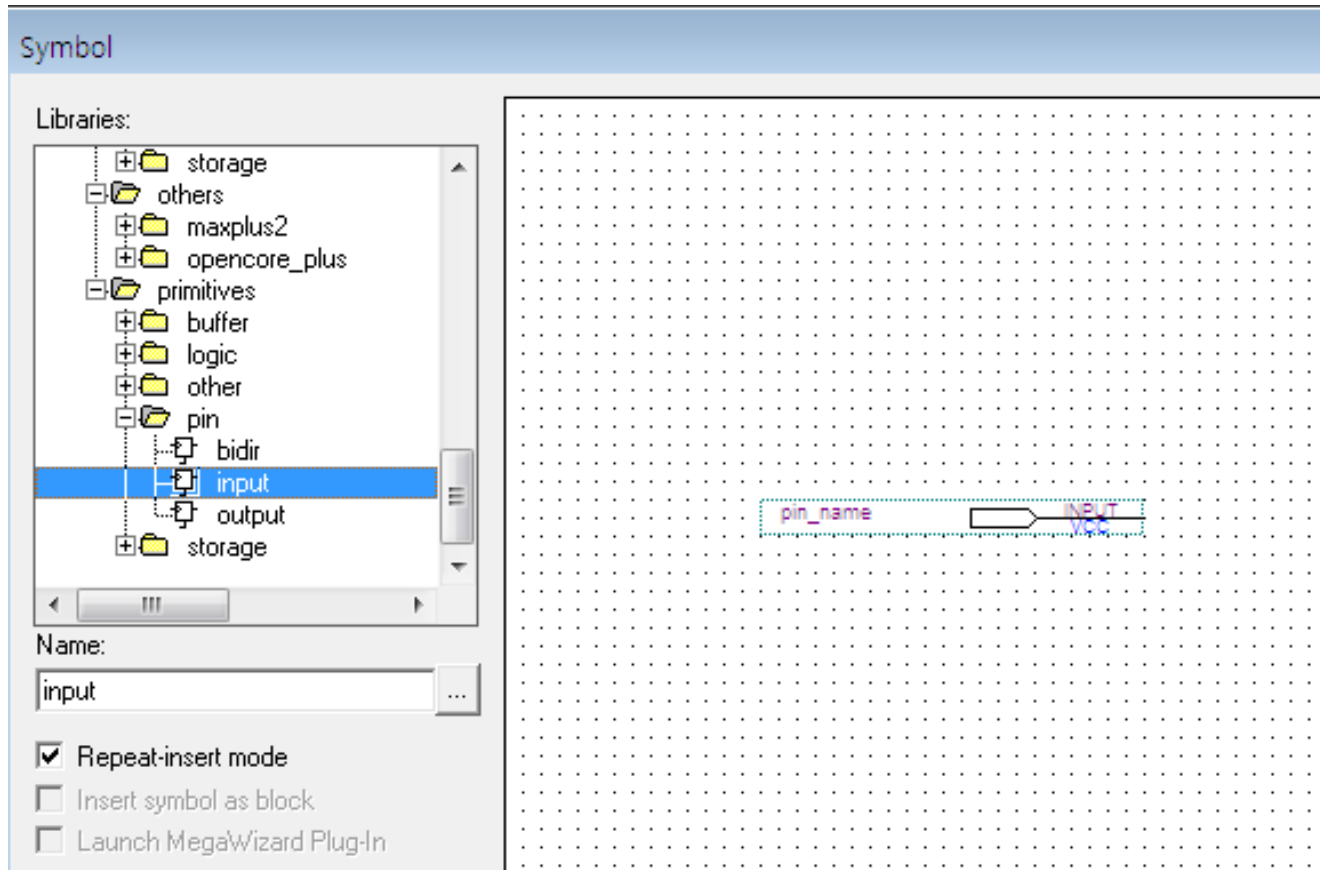➤ Create input / output pin using lpm symbol manager




- Check and set symbol port properties

The image shows a 'Symbol Properties' dialog box with four tabs: General, Ports, Parameters, and Format. The 'Ports' tab is active. It contains a 'Port' section with fields for Name (data[3..0]), Status (Used), Type (INPUT), and Alias (data[3..0]). There are also radio buttons for Inversion (None, All, Pattern) and a 'Binary' dropdown. A 'Change' button is present. Below this is a table of 'Existing ports' with columns: Name, Alias, Inversion, Status, Direction, and Hide Alias. The table lists three ports: data[3..0], gate, and q[3..0]. At the bottom are two buttons: '확인' (OK) and '취소' (Cancel).

Name	Alias	Inversion	Status	Direction	Hide Alias
data[3..0]	data[3..0]	None	Used	INPUT	No
gate	gate	None	Used	INPUT	No
q[3..0]	q[3..0]	None	Used	OUTPUT	No

After creating the symbol, you can see the set information by entering the attribute of the block.


➤ Connection between block and input

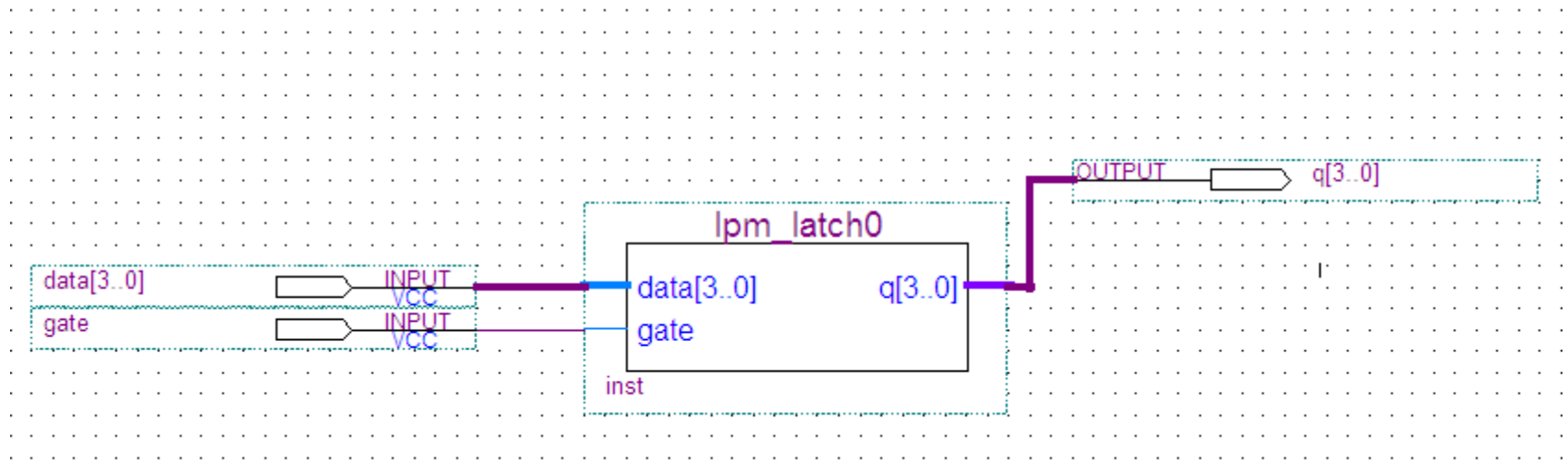


```

ENTITY lpm_latch0 IS
  PORT
  (
    data      : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    gate      : IN STD_LOGIC ;
    q         : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)
  );
END lpm_latch0;

```


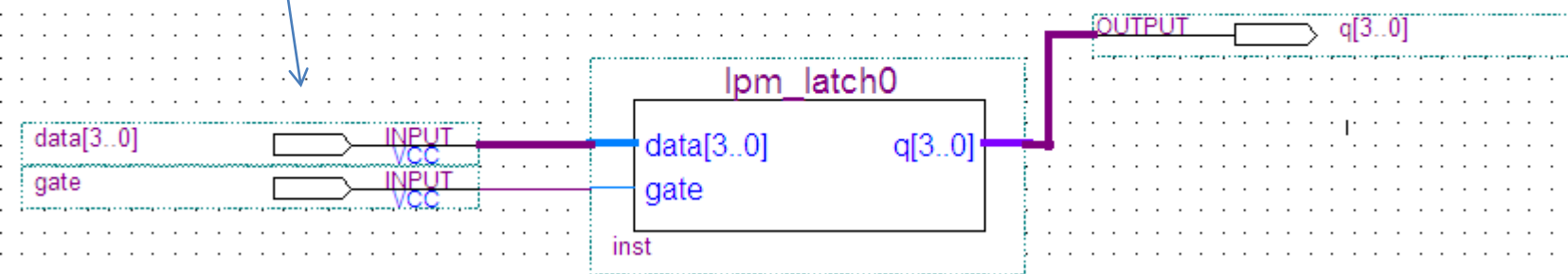


➤ Lpm_counter

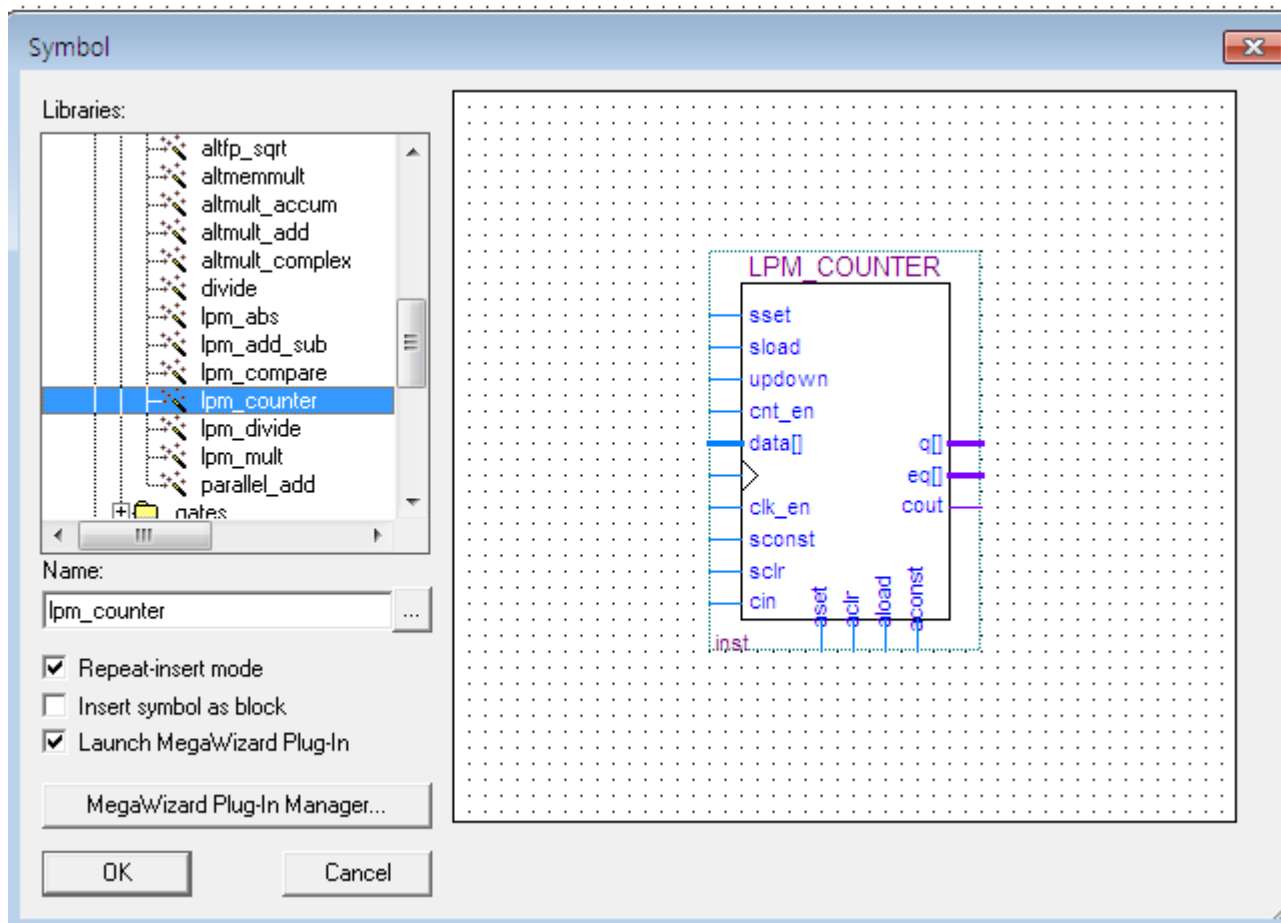

➤ Create a clock divide counter



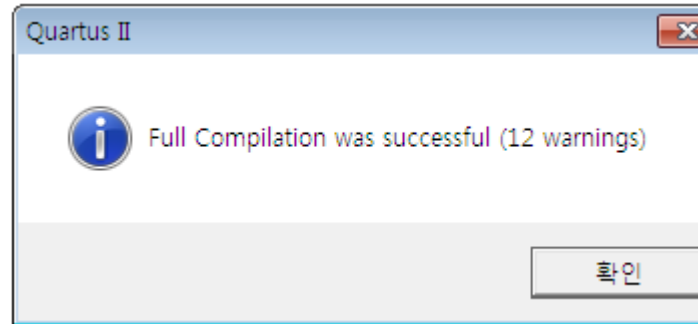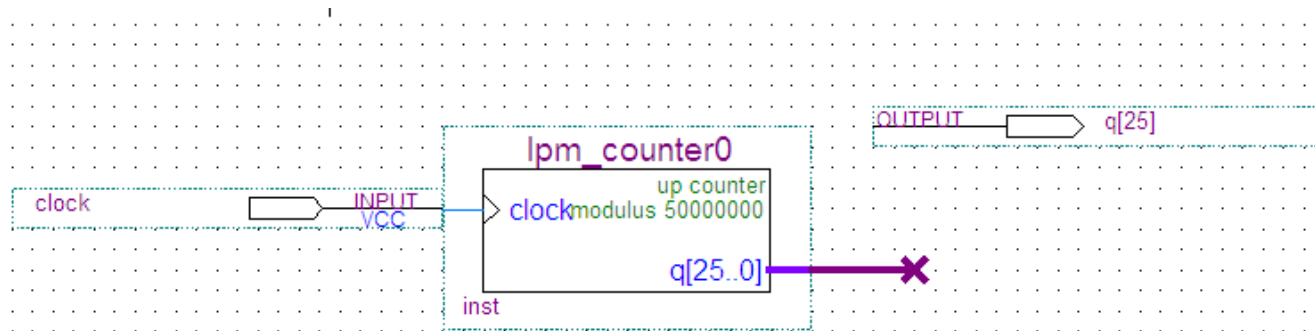

A counter that divides the internal frequency of 50MHz is needed.




The division ratio for switching from 50 MHz to 1 Hz is 50 million.

So to get a 1Hz waveform with a duty ratio of 50%, set the count value to $50,000 / 2 - 1 = 24,999,999$. This count value is 0x17D 783F in hexadecimal, and is 25 bits.

➤ 핀 포팅후 재 컴파일

Edit: X ✓ PIN_N2						
	From	To	Assignment Name	Value	Enabled	
1			Partition Hierarchy	root_partition	Yes	
2		 clock	Location	PIN_N2	Yes	
3		 q[25]	Location	PIN_AE22	Yes	
4		 q	Location		Yes	
5	<<new>>	<<new>>	<<new>>			

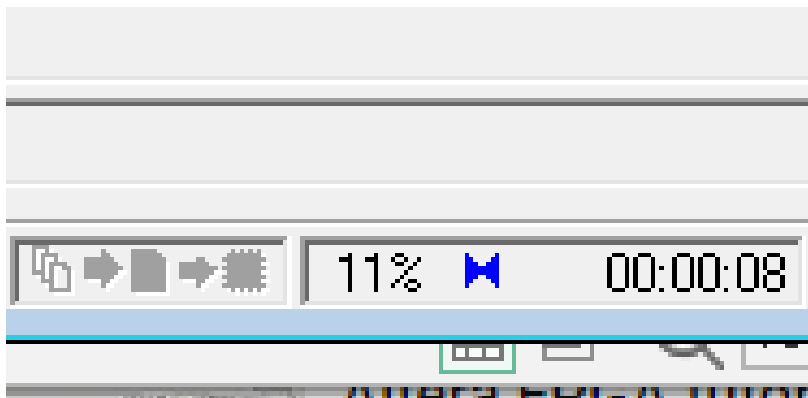


➤ Result of a clock divide counter




➤ Stopwatch primary block schematic

클럭 분주는
26비트 카운
터사용

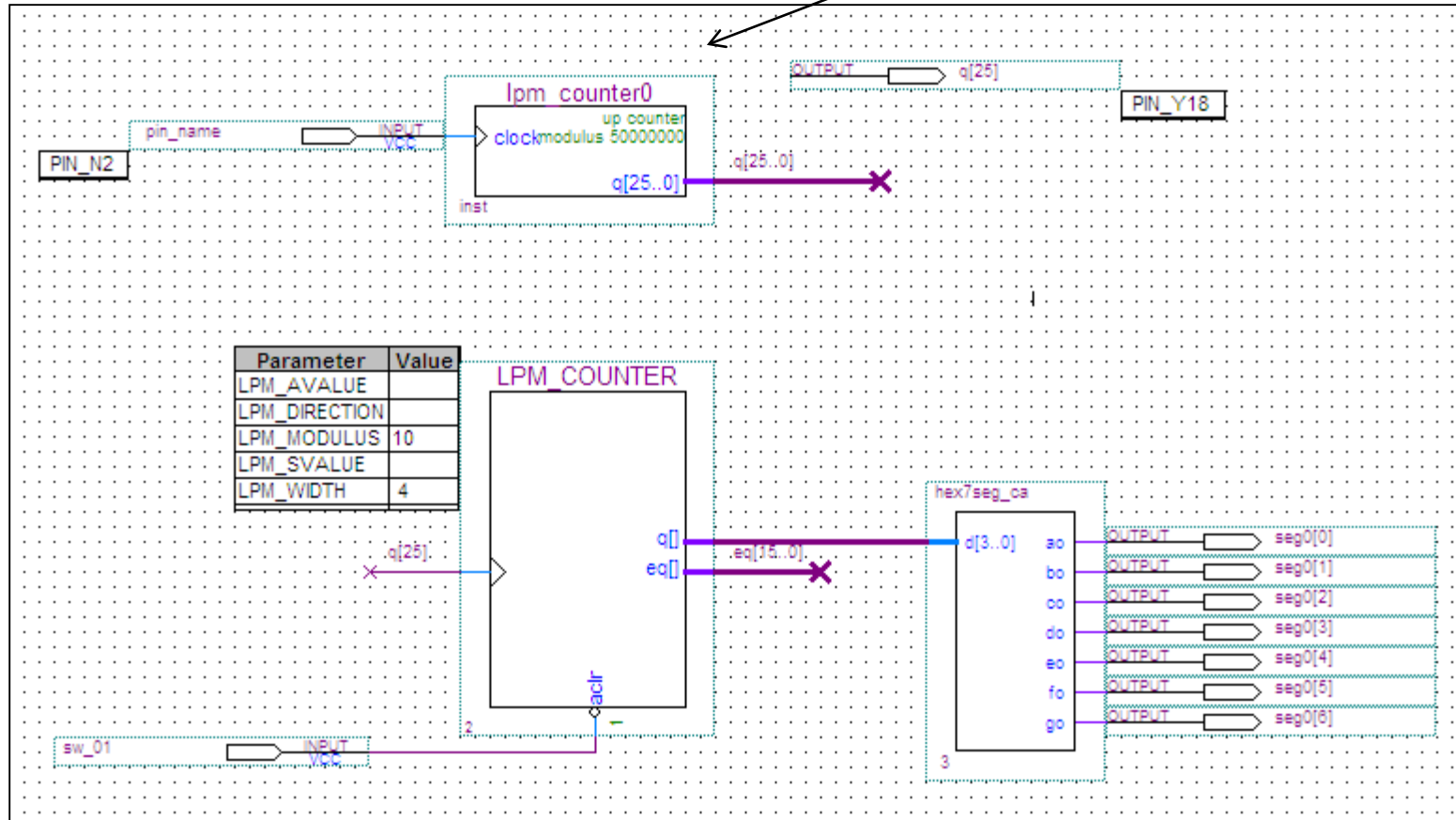

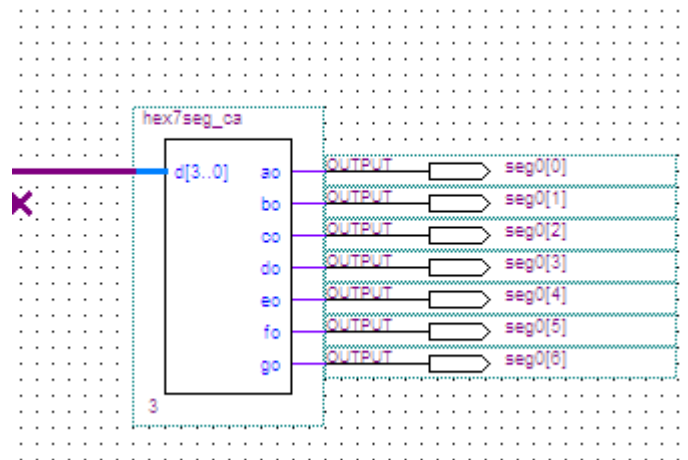➤ Segment controller block production for segment manipulation







```

ARCHITECTURE seven_segment OF hex7seg_ca IS
    SIGNAL input : STD_LOGIC_VECTOR (3 downto 0);
    SIGNAL output: STD_LOGIC_VECTOR (6 downto 0);
BEGIN
    WITH d SELECT
        output <=
            "0000001" WHEN "0000", -- display 0
            "1001111" WHEN "0001", -- display 1
            "0010010" WHEN "0010", -- display 2
            "0000110" WHEN "0011", -- display 3
            "1001100" WHEN "0100", -- display 4
            "0100100" WHEN "0101", -- display 5
            "0100000" WHEN "0110", -- display 6 (with tail)
            "0001111" WHEN "0111", -- display 7
            "0000000" WHEN "1000", -- display 8
            "0000100" WHEN "1001", -- display 9 (with tail)
            "0001000" WHEN "1010", -- display A
            "1100000" WHEN "1011", -- display b
            "0110001" WHEN "1100", -- display C
            "1000010" WHEN "1101", -- display d
            "0110000" WHEN "1110", -- display E
            "0111000" WHEN "1111", -- display F
            "1111111" WHEN others;


```


➤ Stopwatch primary block Result

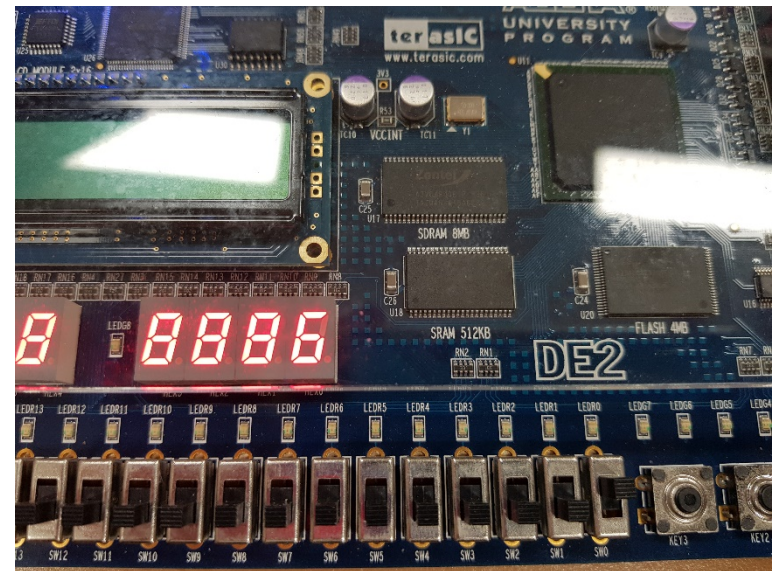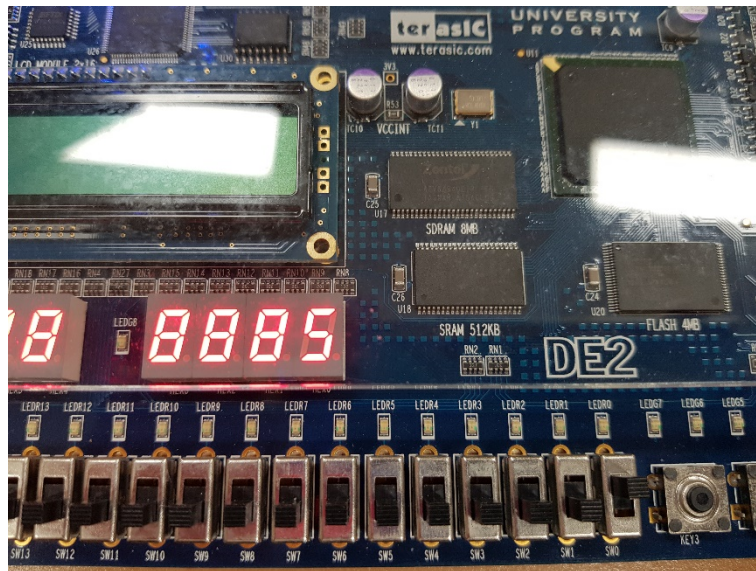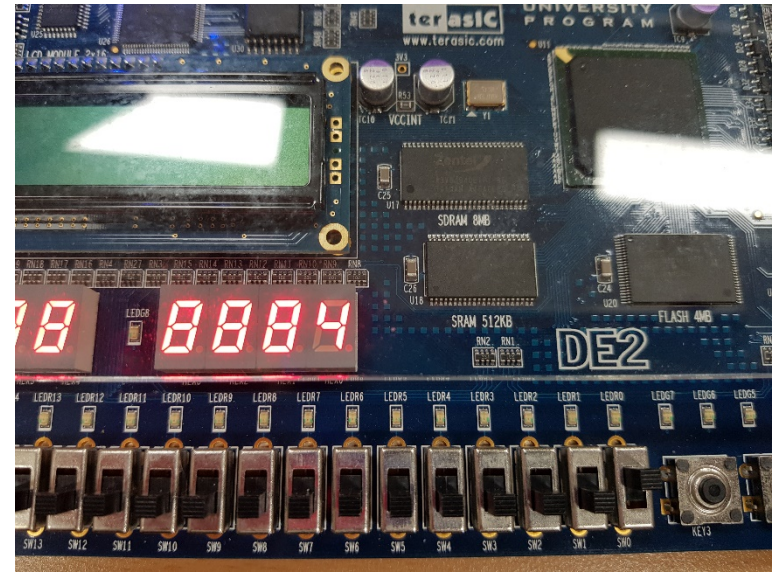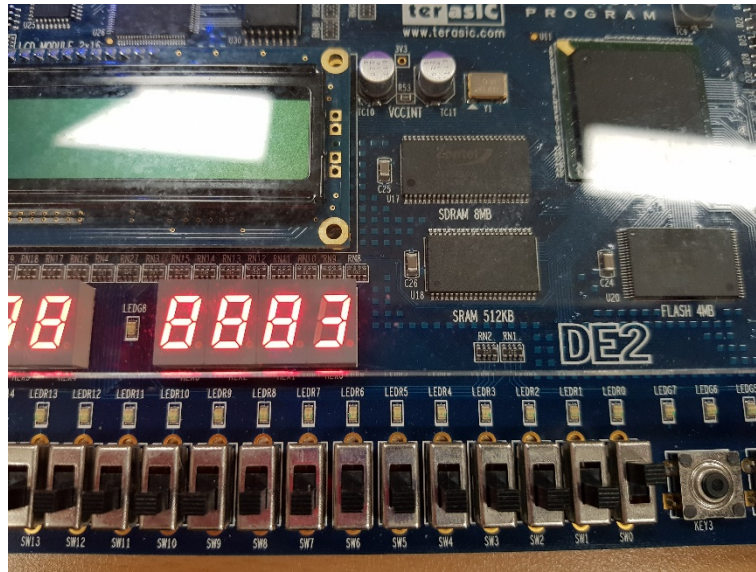

➤ Stopwatch Secondary Block Schematic



SEGMENT

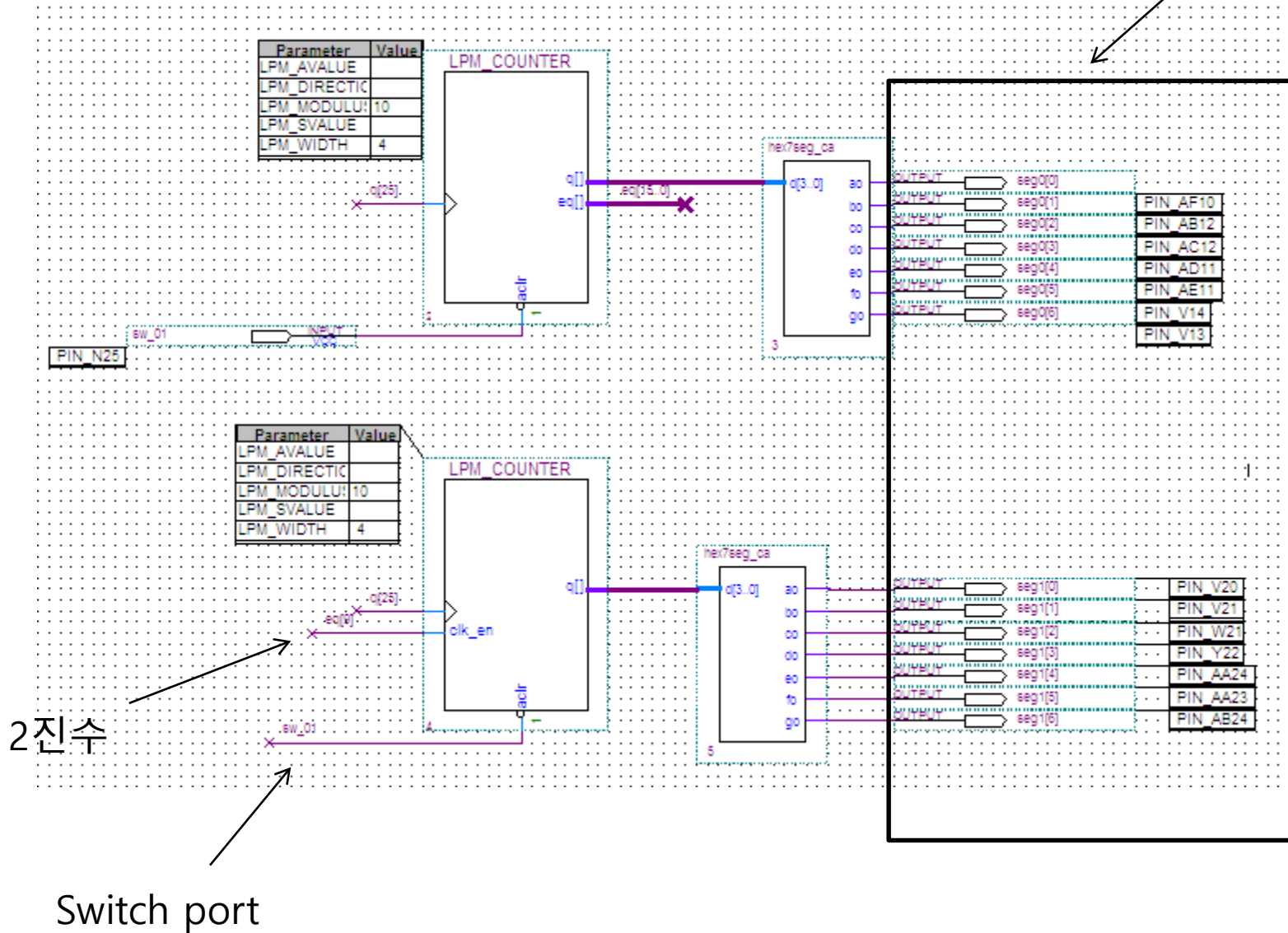

➤ Stopwatch Secondary Block Port Mapping

	Partition Hierarchy	root_partition	Yes
pin_name	Location	PIN_N2	Yes
q[25]	Location	PIN_Y18	Yes
seg0[0]	Location	PIN_AF10	Yes
seg0[1]	Location	PIN_AB12	Yes
seg0[2]	Location	PIN_AC12	Yes
seg0[3]	Location	PIN_AD11	Yes
seg0[4]	Location	PIN_AE11	Yes
seg0[5]	Location	PIN_V14	Yes
seg0[6]	Location	PIN_V13	Yes
sw_01	Location	PIN_N25	Yes
seg1[0]	Location	PIN_V20	Yes
seg1[1]	Location	PIN_V21	Yes
seg1[2]	Location	PIN_W21	Yes
seg1[3]	Location	PIN_Y22	Yes
seg1[4]	Location	PIN_AA24	Yes
seg1[5]	Location	PIN_AA23	Yes
seg1[6]	Location	PIN_AB24	Yes

➤ Result of Stopwatch secondary block

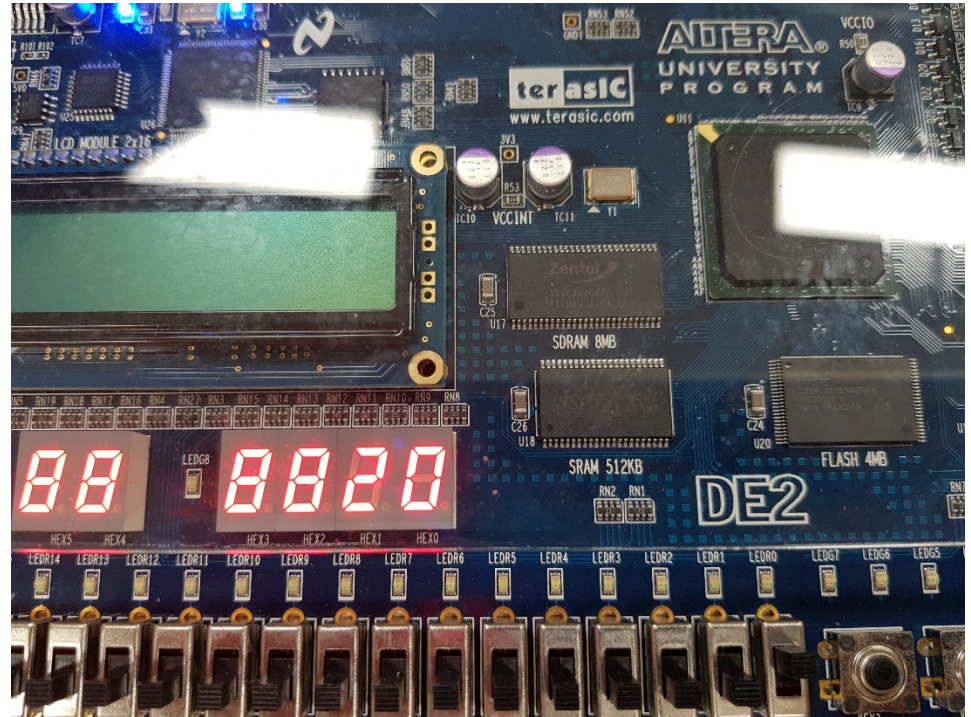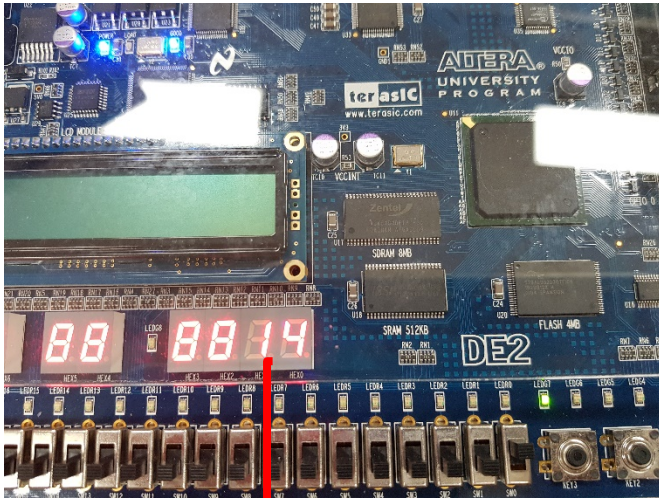

If 0-9 is counted, the decimal segment is additionally marked
Therefore, a two-digit decimal stopwatch display was possible.

Thank you