

# Time Division Multiplexing


석사: 박 제 창(JAICHANGPARK)

20181017-24
 
# 목표

- DE2 Board를 활용한 시분할 멀티플렉싱 구현
- 송신부 클럭 기반 시분할 멀티플렉싱 구현
- 수신부 클럭 기반 시분할 멀티플렉싱 구현
- (단 클럭 신호는 DE2보드 내부 발진기 클럭을 사용한다.)



- **시분할 다중화**(Time Division Multiplexing, **TDM**)이란 전송로를 점유하는 시간을 분할하여 한 개의 전송로에 여러 개의 가상 경로를 구성하는 통신 방식이다.



기본적인 멀티플렉싱 구조도

# Time Division Multiplexing

## Block diagram of TDM system

 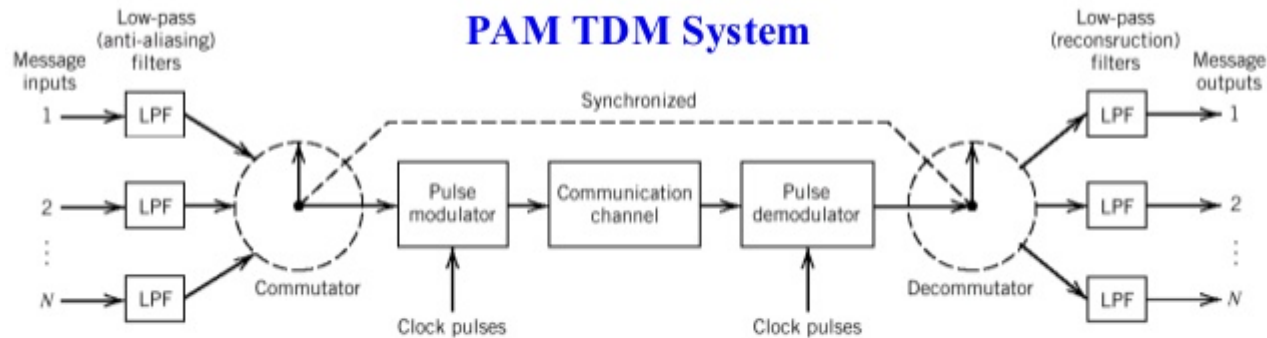

## A Typical Framing Structure for TDM




23

출처:

<https://www.google.co.kr/url?sa=i&source=images&cd=&cad=rja&uact=8&ved=2ahUKEwiCt4Gpip3eAhWJyrwKHS0YC-UQjhx6BAgBEAM&url=https%3A%2F%2Fwww.slideshare.net%2FSpanditLenka%2Ftime-division-multiplexing-77643125&psig=AOvVaw3yyDfHLUmYrjPoAcsHIY7N&ust=1540401869378521>

# Time Division Multiplexing

## ➤ 클럭부 (송, 수신부 공통 사용)

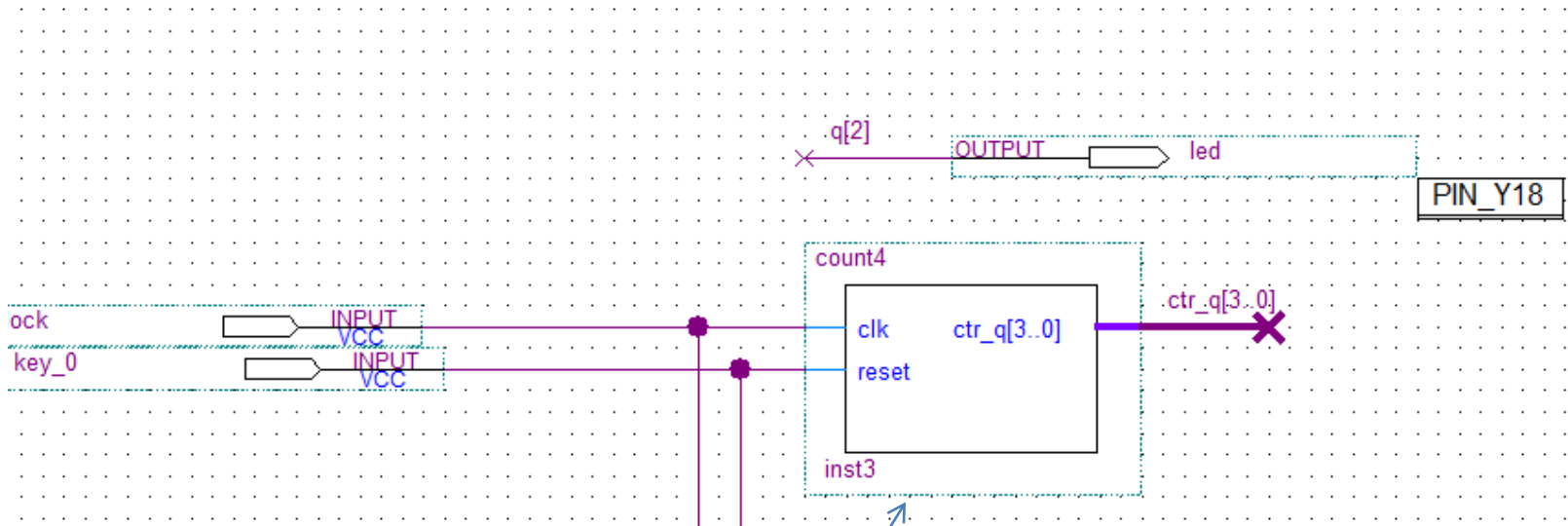

입력 클럭 신호 4분주

# Time Division Multiplexing

## ➤ 클럭부

```
-- count4.vhd
-- Four-bit binary counter based on a component
--   from the Library of Parameterized Modules (LPM)
-- Counter has an active-LOW reset

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
LIBRARY lpm;
USE lpm.lpm_components.ALL;


ENTITY count4 IS
  PORT (
    clk, reset : IN    STD_LOGIC;
    ctr_q      : OUT   STD_LOGIC_VECTOR (3 downto 0));
END count4;

ARCHITECTURE count OF count4 IS
  SIGNAL clrn : STD_LOGIC;
BEGIN
  -- Instantiate 5-bit counter
  clock_divider: lpm_counter
    GENERIC MAP (LPM_WIDTH => 4)
    PORT MAP ( clock => clk,
               aclr  => clrn,
               q     => ctr_q(3 DOWNTO 0));

  clrn  <= not reset;
END count;
```

# Time Division Multiplexing

## ➤ 송신부 디코더 설계

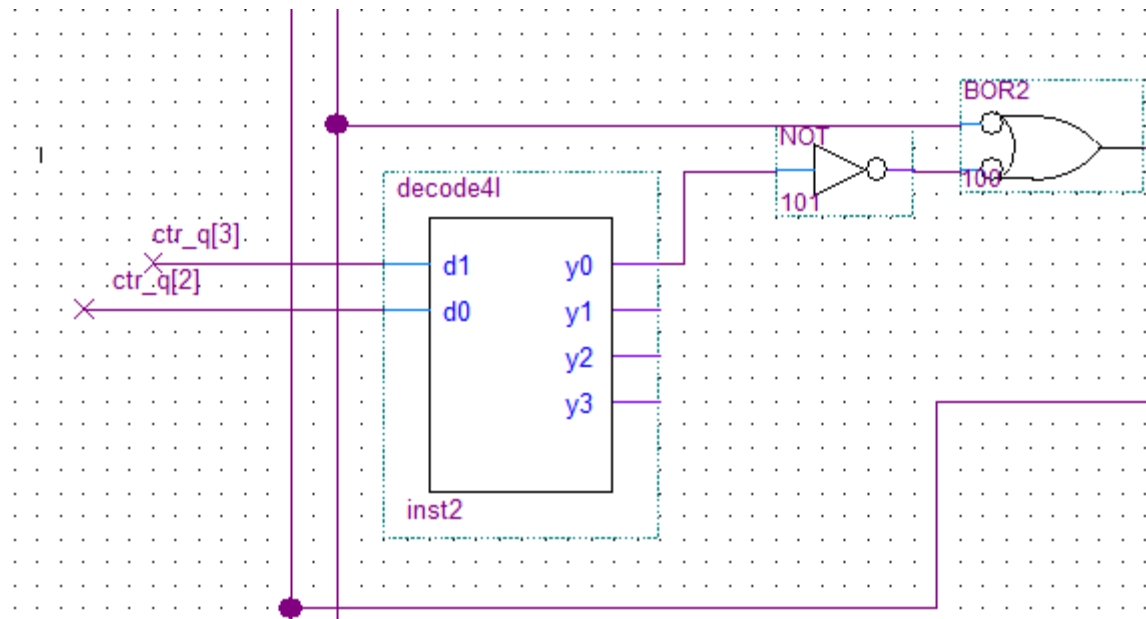

## Time Division Multiplexing

### ➤ 송신부 디코더 설계

```
ENTITY decode41 IS
PORT (
    d1, d0 : IN BIT;
    y0, y1, y2, y3: OUT BIT);
END decode41;


ARCHITECTURE a of decode41 IS
    SIGNAL inputs : BIT_VECTOR(1 downto 0);
    SIGNAL outputs: BIT_VECTOR(0 to 3);
BEGIN
    inputs <= d1 & d0;
    WITH inputs SELECT
        outputs <= "0111" WHEN "00",
                  "1011" WHEN "01",
                  "1101" WHEN "10",
                  "1110" WHEN "11";

    y0 <= outputs(0);
    y1 <= outputs(1);
    y2 <= outputs(2);
    y3 <= outputs(3);
end a;
```



# Time Division Multiplexing

## ➤ 송신부 4비트 시프터 설계

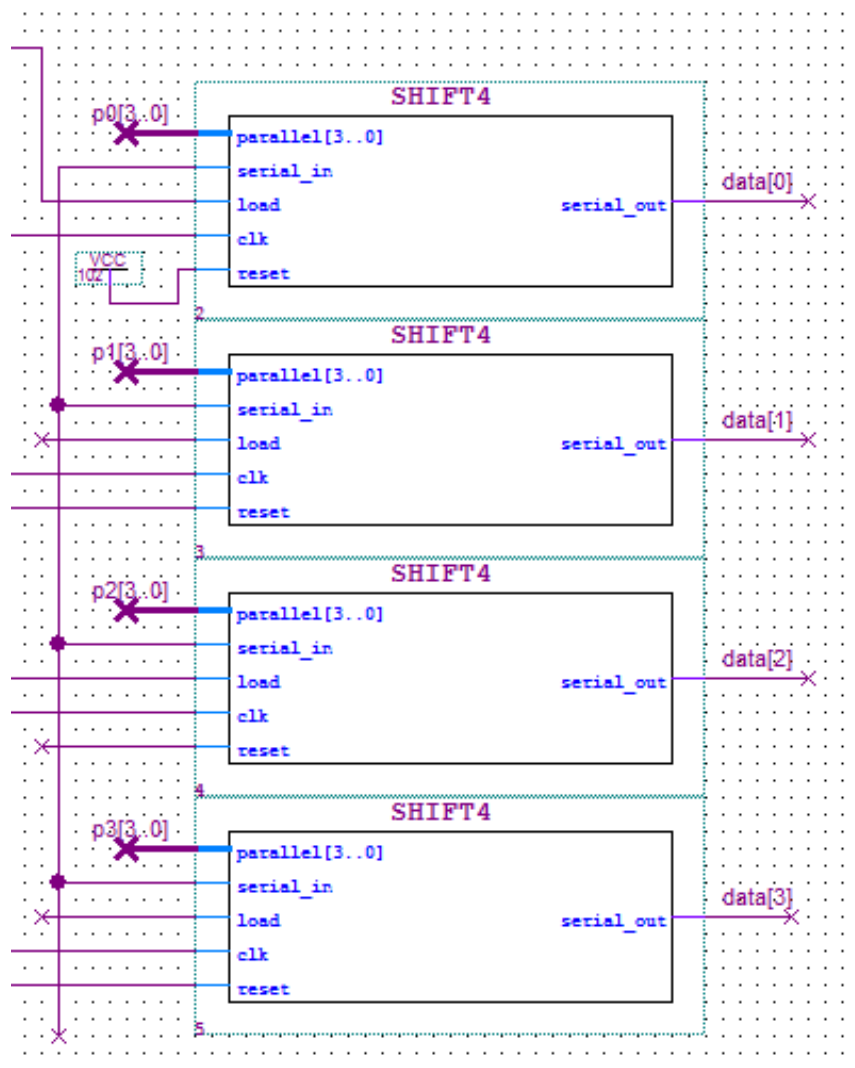

## Time Division Multiplexing

### ➤ 송신부 4비트 시프터 설계

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
LIBRARY lpm;
USE lpm.lpm_components.ALL;

ENTITY shift4 IS
    PORT(
        parallel      : IN    STD_LOGIC_VECTOR(3 downto 0);
        serial_in     : IN    STD_LOGIC      := '0';
        load, clk, reset : IN    STD_LOGIC;
        serial_out     : OUT   STD_LOGIC);
END shift4;


ARCHITECTURE shift OF shift4 IS
    SIGNAL clrn: STD_LOGIC;
BEGIN
    -- Instantiate 4-bit shift register
    four_bit_shift: lpm_shiftreg
        GENERIC MAP (LPM_WIDTH => 4, LPM_DIRECTION => "RIGHT")
        PORT MAP ( aclr      => clrn,
                   clock    => clk,
                   load     => load,
                   --
                   shiftin  => serial_in,
                   data     => parallel(3 downto 0),
                   shiftout  => serial_out);

    clrn    <= not reset;
END shift;
```

# Time Division Multiplexing

- 1차 핀 설정
 
## Top View - Wire Bond Cyclone II - EP2C35F672C6



# Time Division Multiplexing

- 1차 핀 설정

Quartus II - C:/Users/5E406/Desktop/bx\_rx/bx\_rx - tx\_rx - [Pin Planner]

File Edit View Processing Tools Window

Groups

Named: [ ]

Node Name	Direction
p0[3..0]	Input
p1[3..0]	Input
p2[3..0]	Input
p3[3..0]	Input
<<new node>>	

Top View - Wire Bond  
Cyclone II - EP2C35F672C6

1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26

A B C D E F G H J K L M N P R T U V W Y AA AB AC AD AE AF

Filter: Pins: all


Node Name	Direction	Location	I/O Bank	VREF Group	I/O Standard	Reserved
a1	Output	PIN_AE23	7	B7_N0	3.3-V LVTTTL (default)	
b1	Output	PIN_AF23	7	B7_N0	3.3-V LVTTTL (default)	
c1	Output	PIN_AB21	7	B7_N0	3.3-V LVTTTL (default)	
clock	Input	PIN_N2	2	B2_N1	3.3-V LVTTTL (default)	
d1	Output	PIN_AC22	7	B7_N0	3.3-V LVTTTL (default)	
key_0	Input	PIN_G26	5	B5_N0	3.3-V LVTTTL (default)	
led	Output	PIN_Y18	7	B7_N0	3.3-V LVTTTL (default)	
p0[3]	Input	PIN_N25	5	B5_N1	3.3-V LVTTTL (default)	
p0[2]	Input	PIN_N26	5	B5_N1	3.3-V LVTTTL (default)	
p0[1]	Input	PIN_P25	6	B6_N0	3.3-V LVTTTL (default)	
p0[0]	Input	PIN_AE14	7	B7_N1	3.3-V LVTTTL (default)	
p1[3]	Input	PIN_AF14	7	B7_N1	3.3-V LVTTTL (default)	
p1[2]	Input	PIN_AD13	8	B8_N0	3.3-V LVTTTL (default)	
p1[1]	Input	PIN_AC13	8	B8_N0	3.3-V LVTTTL (default)	

For Help, press F1

NUM

# Time Division Multiplexing



- 1차 회로 구성

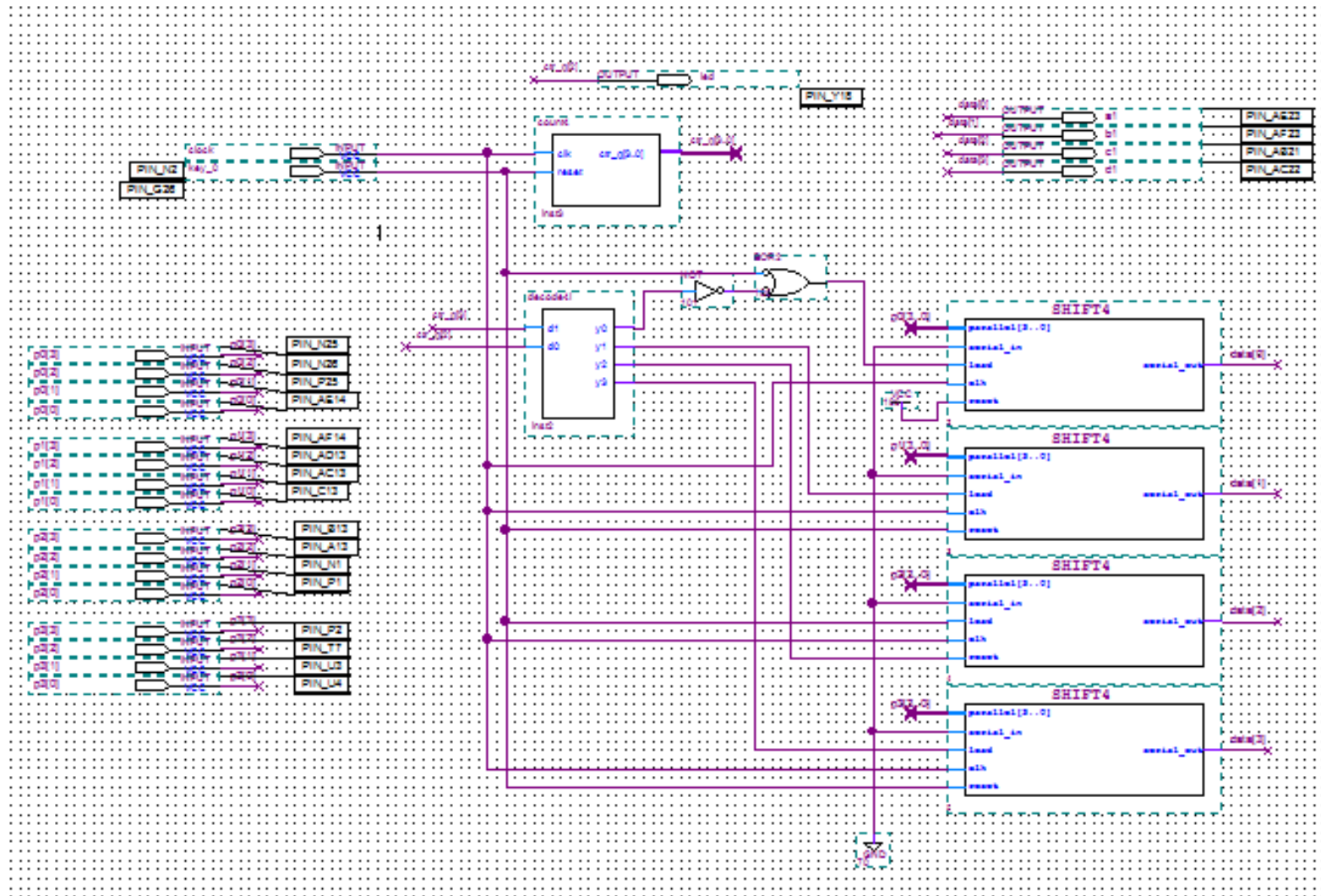
 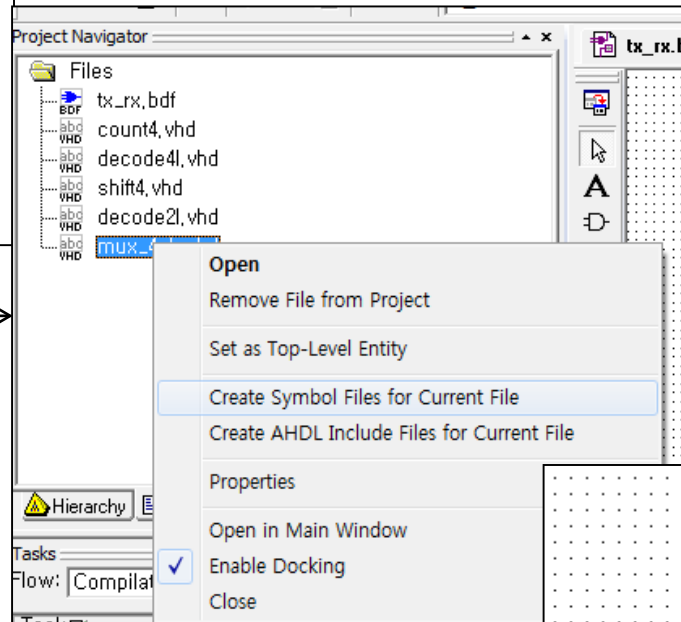
# Time Division Multiplexing


```
ENTITY mux_4ch IS
  PORT (
    s : IN    BIT_VECTOR (1 downto 0);
    d : IN    BIT_VECTOR (3 downto 0);
    y : OUT   BIT);
END mux_4ch;

ARCHITECTURE a OF mux_4ch IS
BEGIN
  -- Selected Signal Assignment
  MUX4: WITH s SELECT
    y <= d(0) WHEN "00",
          d(1) WHEN "01",
          d(2) WHEN "10",
          d(3) WHEN "11";
END a;
```



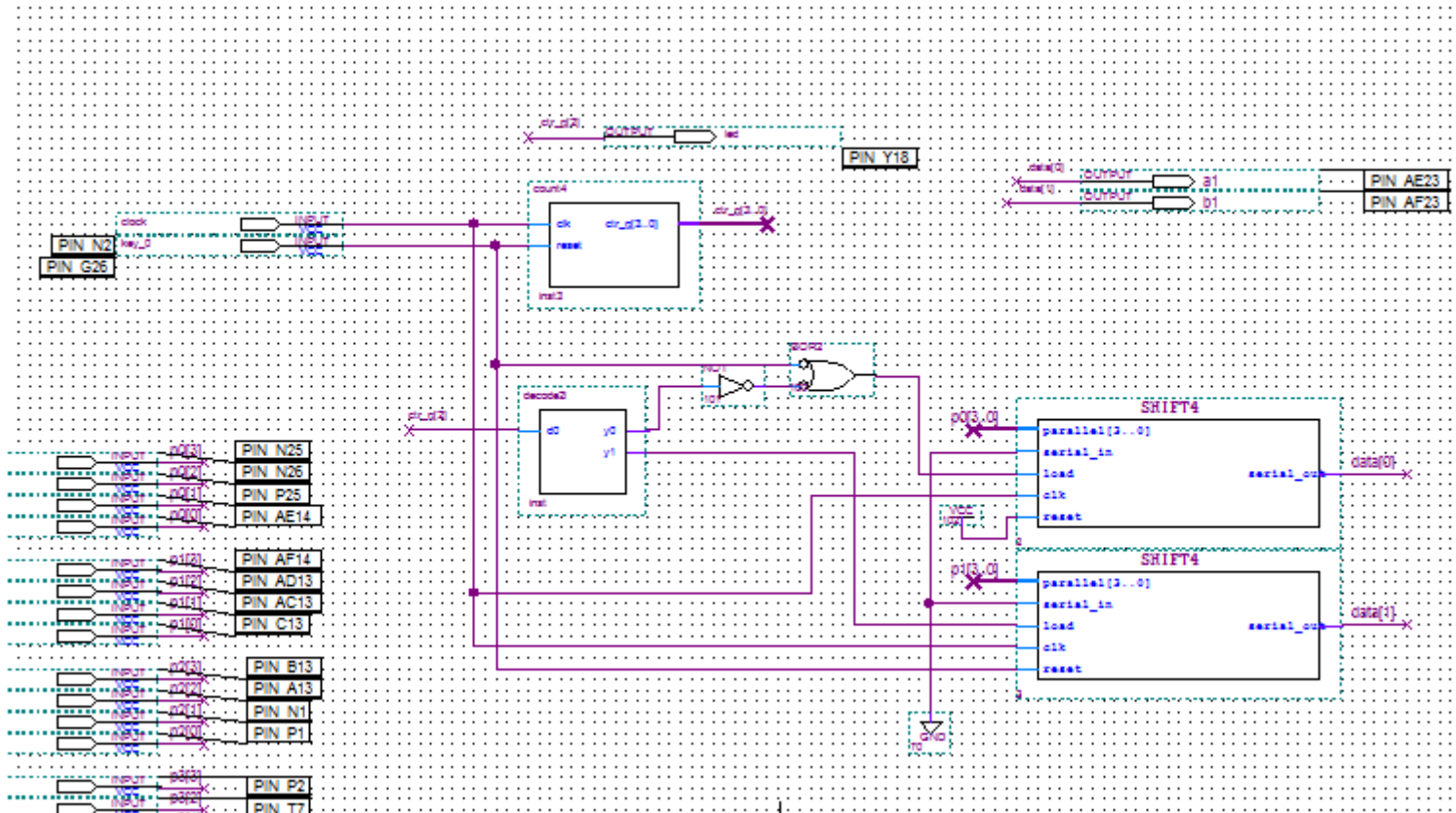
# Time Division Multiplexing

Led수 부족으로 다음과 같이 시프트 레지스터 개수를 줄이고 디코더 개수 또한 줄임.



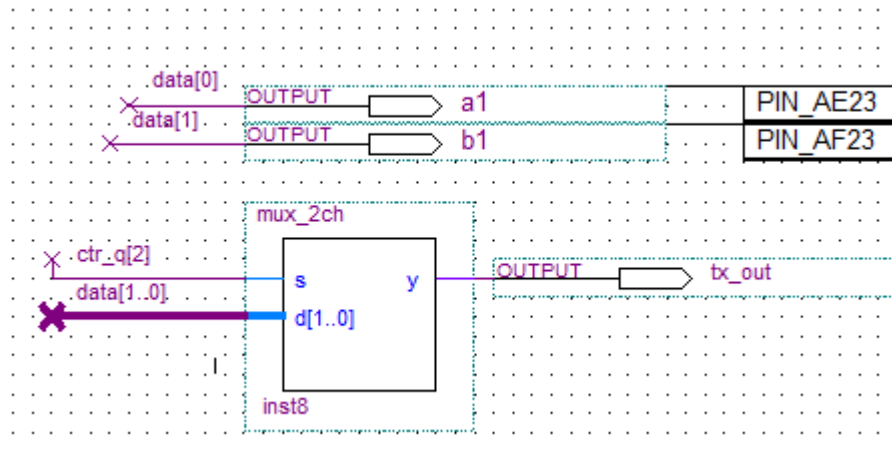
# Time Division Multiplexing

```
1  ENTITY mux_2ch IS
2  PORT (
3      s : IN    BIT;
4      d : IN    BIT_VECTOR (1 downto 0);
5      y : OUT   BIT);
6  END mux_2ch;
7
8  ARCHITECTURE a OF mux_2ch IS
9  BEGIN
10     -- Selected Signal Assignment
11     MUX2: WITH s SELECT
12         y <= d(0) WHEN '0',
13             d(1) WHEN '1';
14
15     END a;
16
17
```






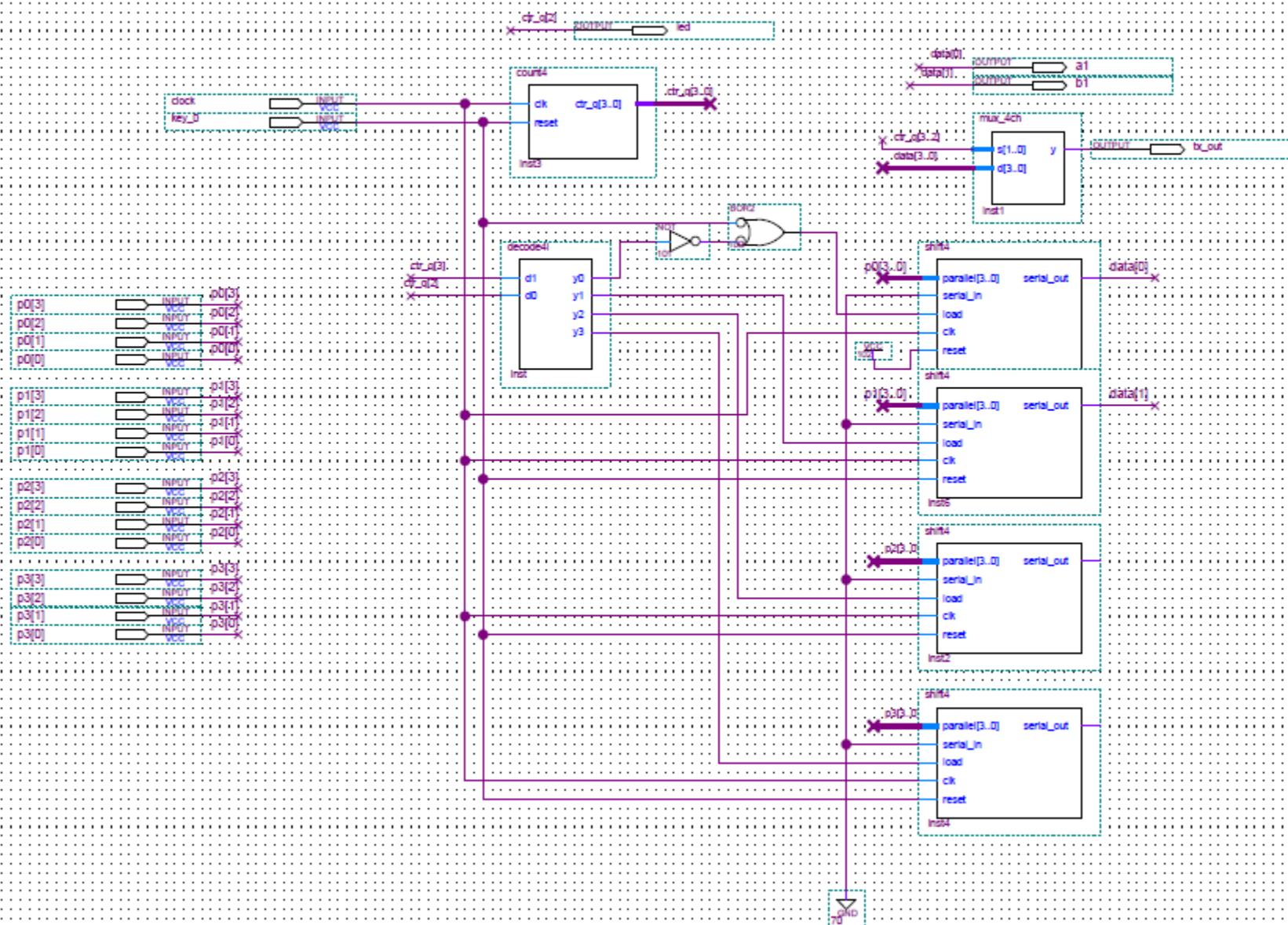

# Time Division Multiplexing

## 수신부 디코더 설계

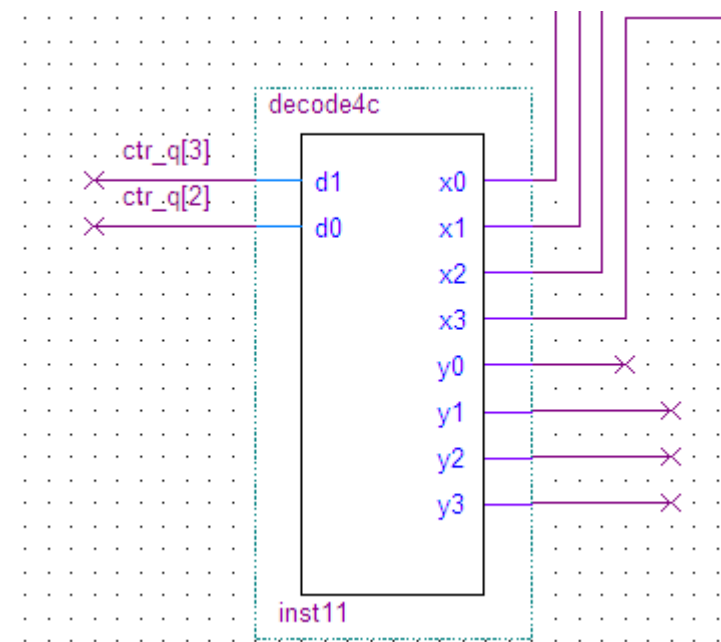

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;


-- Define inputs and outputs
ENTITY decode4c IS
    PORT (
        d1, d0 : IN STD_LOGIC;
        x0, x1, x2, x3, y0, y1, y2, y3 : OUT STD_LOGIC);
END decode4c;

-- Define i/o relationship
ARCHITECTURE four_ch_decode OF decode4c IS
    BEGIN
        -- Concurrent Signal Assignment
        x0 <= (not d1) and (not d0); -- input 00: output x0 HIGH
        x1 <= (not d1) and ( d0); -- input 01: output x1 HIGH
        x2 <= ( d1) and (not d0); -- input 10: output x2 HIGH
        x3 <= ( d1) and ( d0); -- input 11: output x3 HIGH

        y0 <= not ((not d1) and (not d0)); -- input 00: output x0 HIGH
        y1 <= not ((not d1) and ( d0)); -- input 01: output x1 HIGH
        y2 <= not (( d1) and (not d0)); -- input 10: output x2 HIGH
        y3 <= not (( d1) and ( d0)); -- input 11: output x3 HIGH
    END four_ch_decode;
```

# Time Division Multiplexing

- 수신부 4비트 시프트 설계

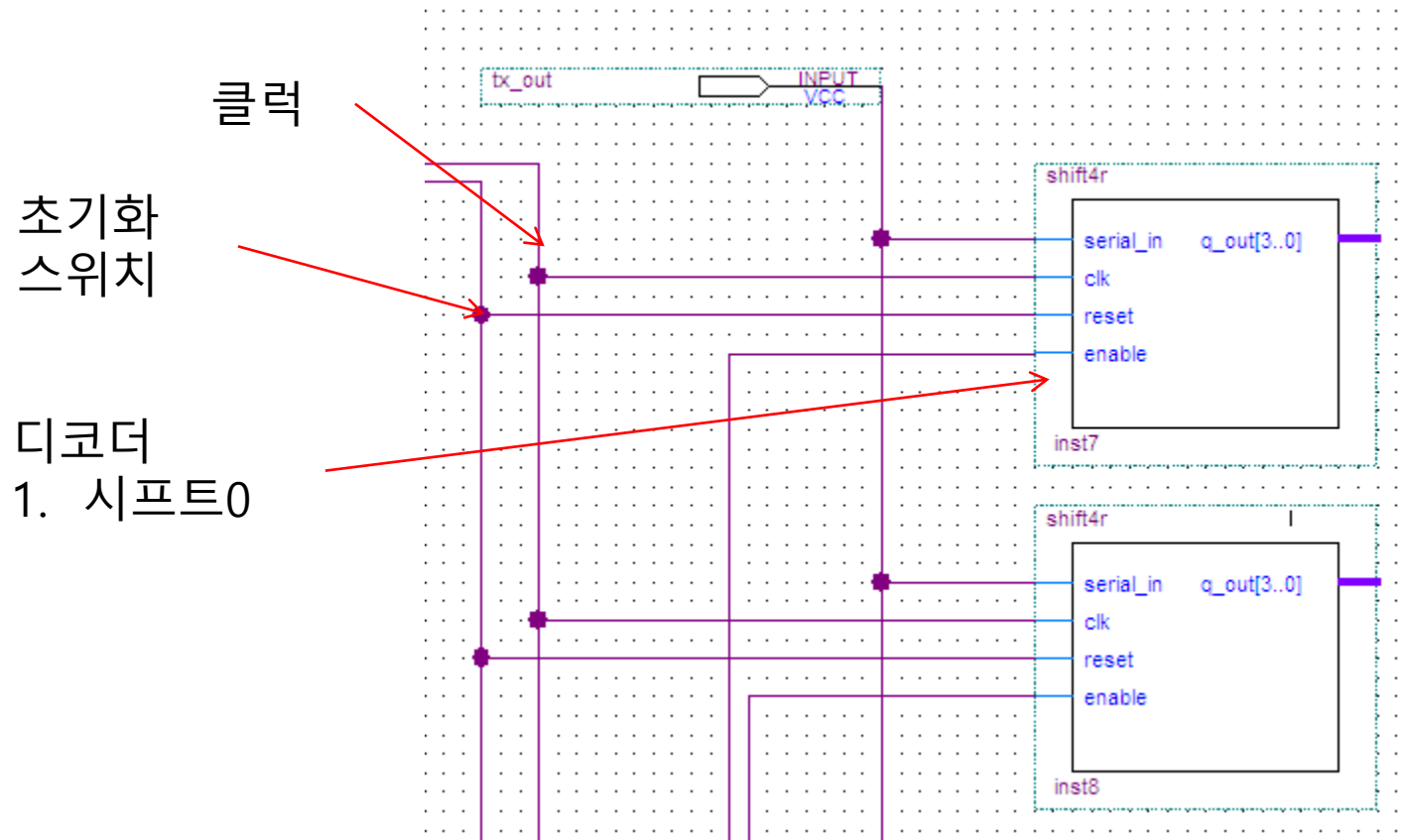

# Time Division Multiplexing

- 수신부 4비트 시프트 설계

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
LIBRARY lpm;
USE lpm.lpm_components.ALL;

-- ENTITY shift4r IS
-- PORT(
--     serial_in      : IN    STD_LOGIC;
--     clk, reset, enable : IN    STD_LOGIC;
--     q_out          : OUT   STD_LOGIC_VECTOR(3 downto 0));
-- END shift4r;


-- ARCHITECTURE shift OF shift4r IS
-- COMPONENT lpm_shiftreg
--     GENERIC (LPM_WIDTH: POSITIVE; LPM_DIRECTION: STRING);
--     PORT (clock: IN STD_LOGIC;
--           enable: IN STD_LOGIC := '1';
--           shiftin: IN STD_LOGIC := '1';
--           aclr: IN STD_LOGIC := '0';
--           q: OUT STD_LOGIC_VECTOR(LPM_WIDTH-1 DOWNT0 0));
-- END COMPONENT;

--     SIGNAL clrn: STD_LOGIC;
-- BEGIN
-- --Instantiate 4-bit shift register
--     four_bit_shift: lpm_shiftreg
--         GENERIC MAP (LPM_WIDTH => 4, LPM_DIRECTION => "RIGHT")
--         PORT MAP (
--             aclr      => clrn,
--             clock      => clk,
--             enable     => enable,
--             shiftin    => serial_in,
--             q          => q_out(3 downto 0));

--     clrn    <= not reset;
-- END shift;
```

# Time Division Multiplexing

## ■ 수신부 레치 설계

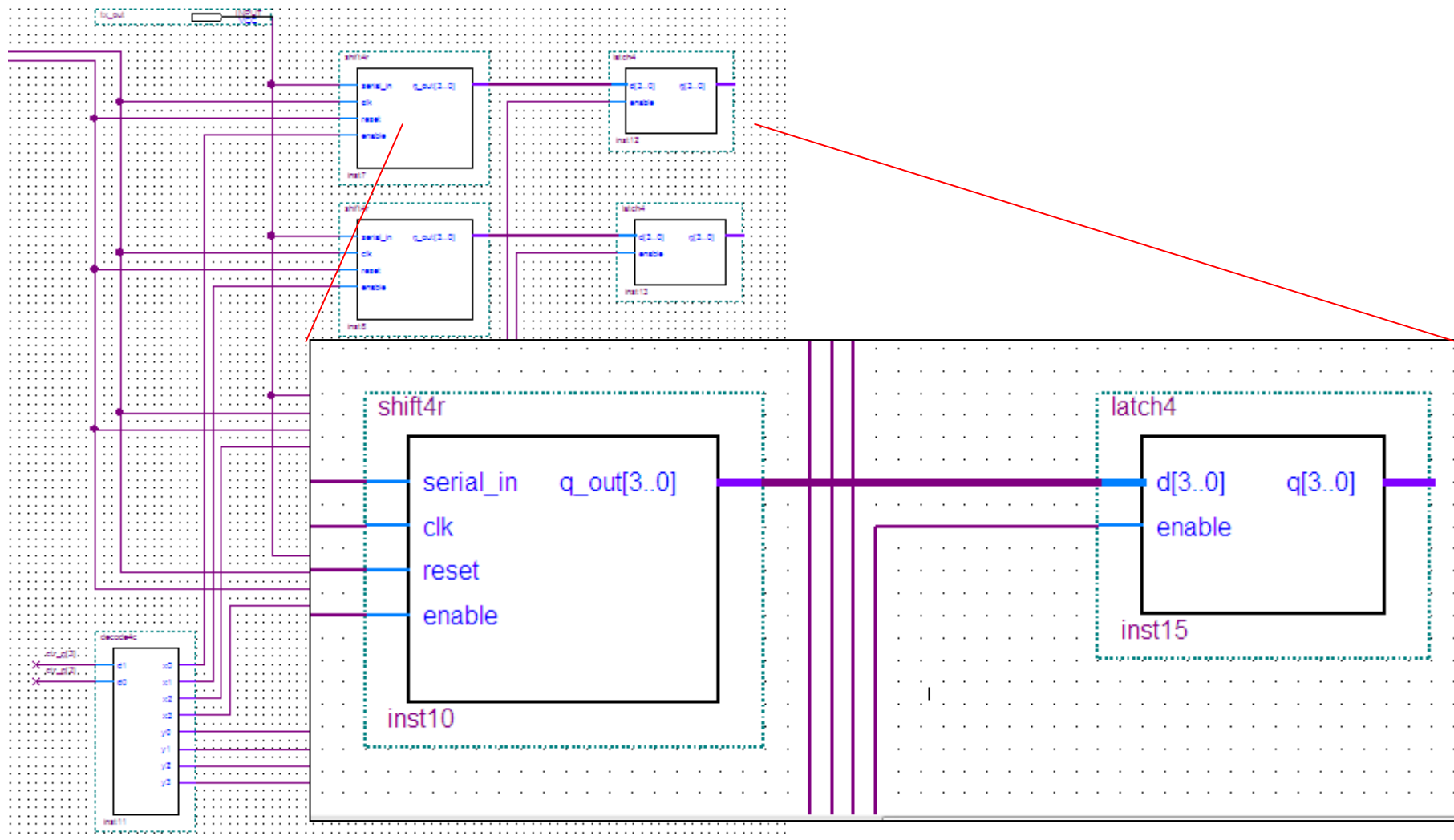


# Time Division Multiplexing

- 수신부 레지 설계

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
LIBRARY lpm;
USE lpm.lpm_components.all;

ENTITY latch4 IS
    PORT (
        d      : IN    STD_LOGIC_VECTOR (3 downto 0);
        enable  : IN    STD_LOGIC;
        q      : OUT   STD_LOGIC_VECTOR (3 downto 0));
END latch4;

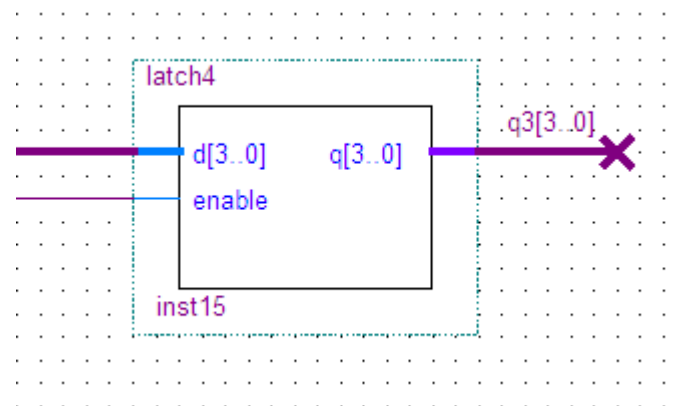
ARCHITECTURE latch OF latch4 IS
BEGIN
    four_bit_latch: lpm_latch
        GENERIC MAP (LPM_WIDTH => 4)
        PORT MAP (data => d(3 downto 0),
                  gate  => enable,
                  q      => q(3 downto 0));
END latch;
```



# Time Division Multiplexing

- 수신부 출력 포트 <- 레치로 부터 나오는 신호

※단일 보드 내에서 동작 확인을  
위한 변수명 변경

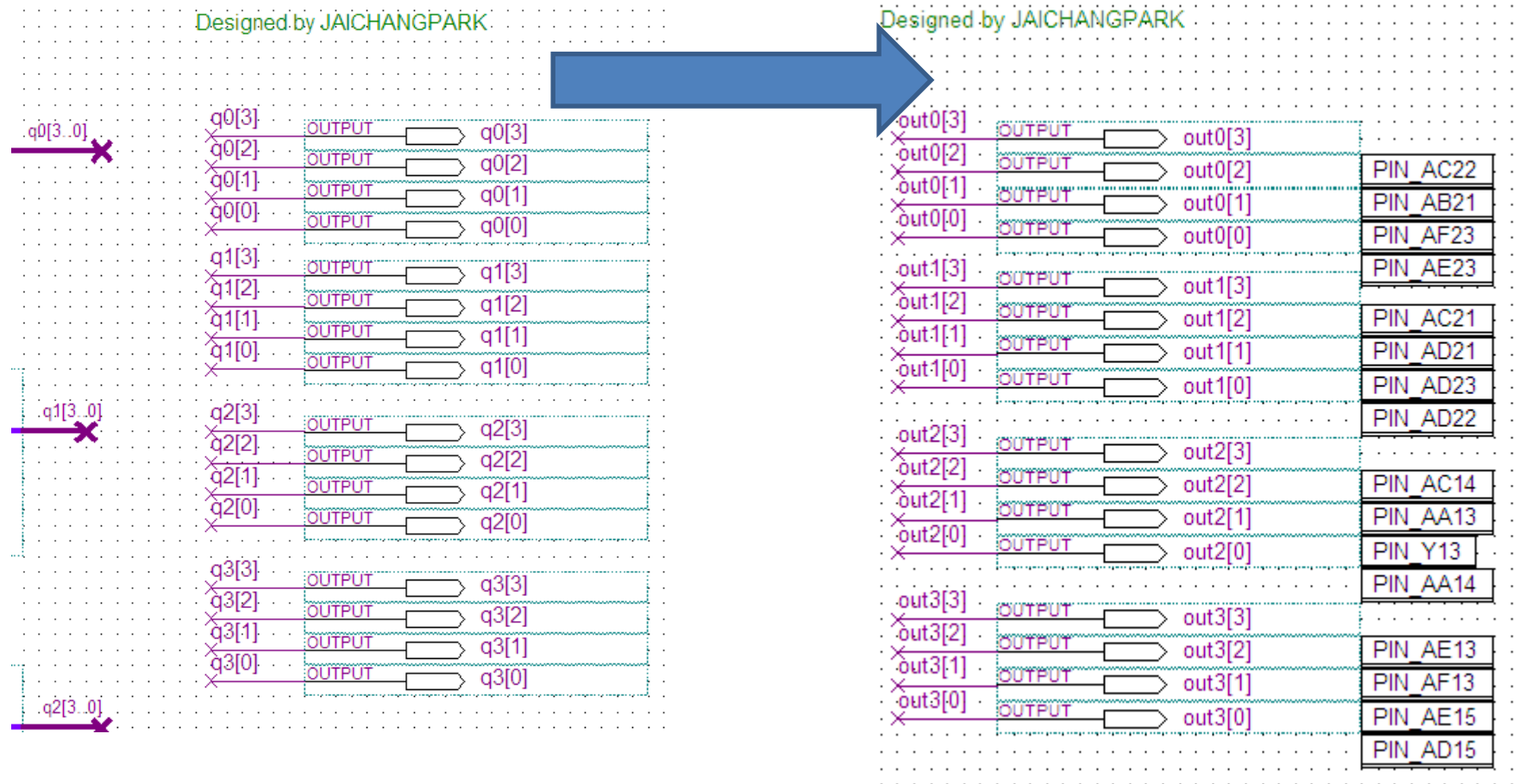


# Time Division Multiplexing

## ▪ De2 포트핀 설정

a1	Location PIN_AE22
b1	Location PIN_AF22
clock	Location PIN_D13
key_0	Location PIN_G26
led	Location PIN_W19
out0[0]	Location PIN_AE23
out0[1]	Location PIN_AF23
out0[2]	Location PIN_AB21
out0[3]	Location PIN_AC22
out1[0]	Location PIN_AD22
out1[1]	Location PIN_AD23
out1[2]	Location PIN_AD21
out1[3]	Location PIN_AC21
out2[0]	Location PIN_AA14
out2[1]	Location PIN_Y13
out2[2]	Location PIN_AA13
out2[3]	Location PIN_AC14
out3[0]	Location PIN_AD15
out3[1]	Location PIN_AE15
out3[2]	Location PIN_AF13
out3[3]	Location PIN_AE13

p0[0]	Location PIN_N25
p0[1]	Location PIN_N26
p0[2]	Location PIN_P25
p0[3]	Location PIN_AE14
p1[0]	Location PIN_AF14
p1[1]	Location PIN_AD13
p1[2]	Location PIN_AC13
p1[3]	Location PIN_C13
p2[0]	Location PIN_B13
p2[1]	Location PIN_A13
p2[2]	Location PIN_N1
p2[3]	Location PIN_P1
p3[0]	Location PIN_P2
p3[1]	Location PIN_T7
p3[2]	Location PIN_U3
p3[3]	Location PIN_U4
tx_out	Location PIN_Y12




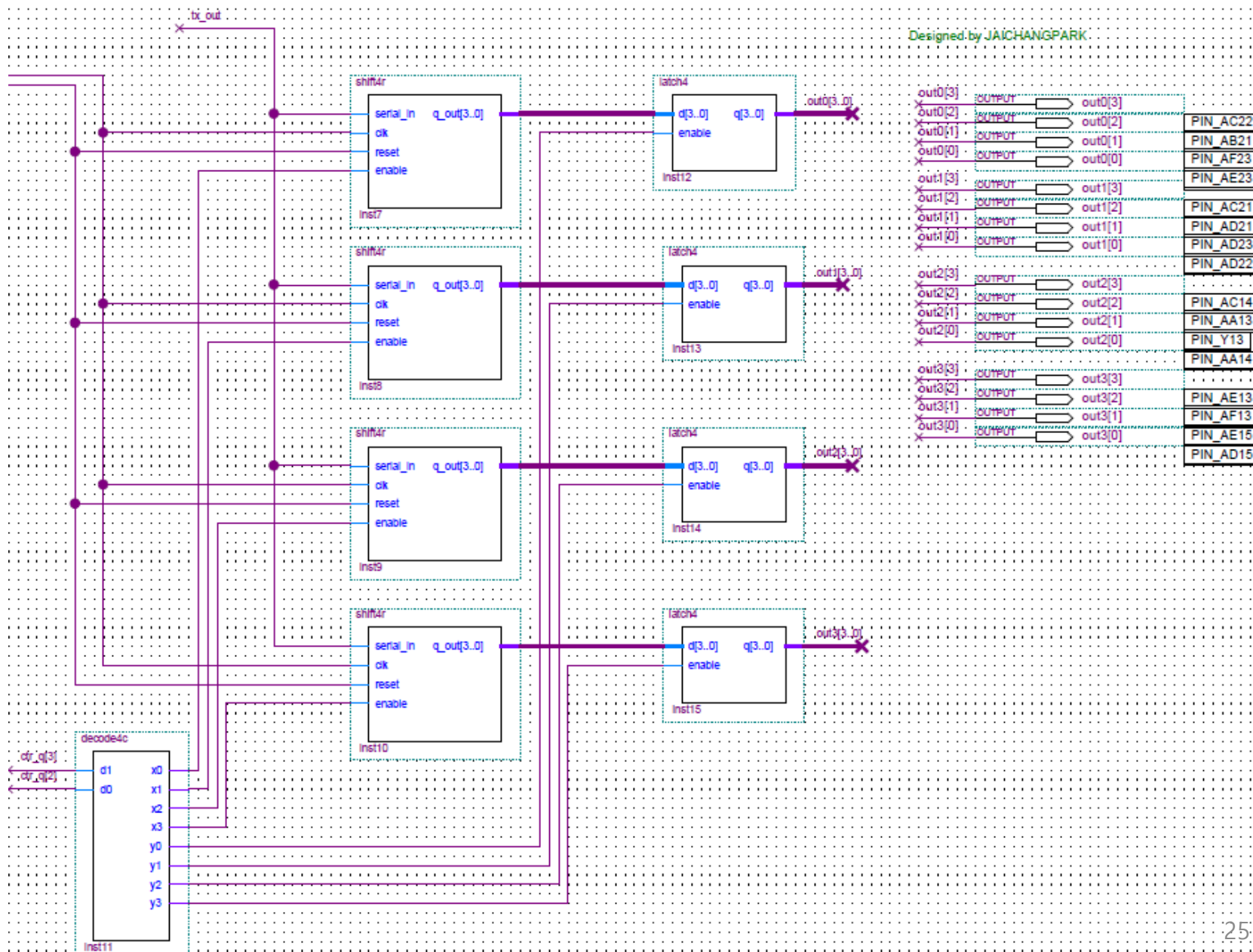

# Time Division Multiplexing


- 전체 회로 구성도

## 송신부

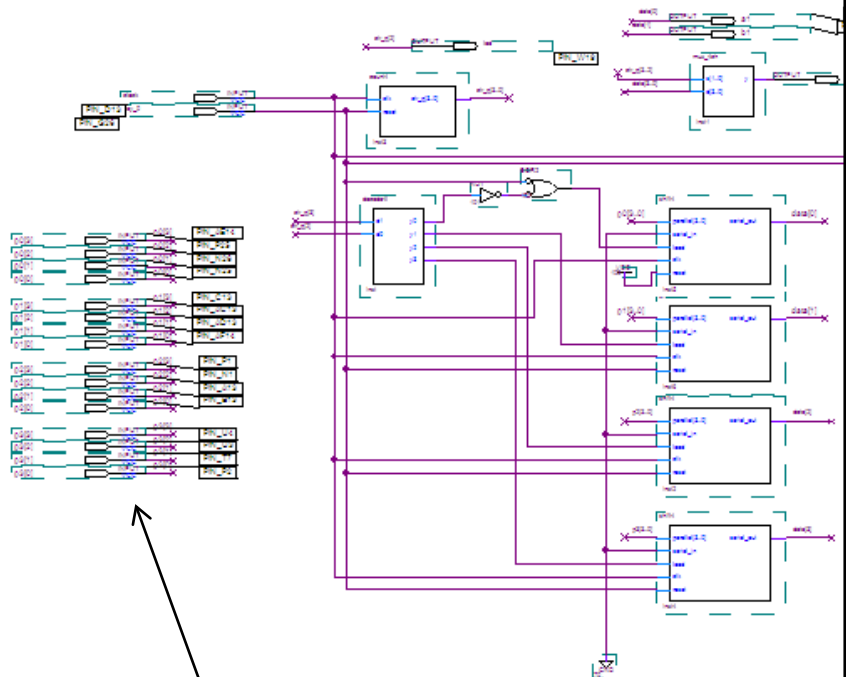

입력 신호 (스위치)

## 수신부

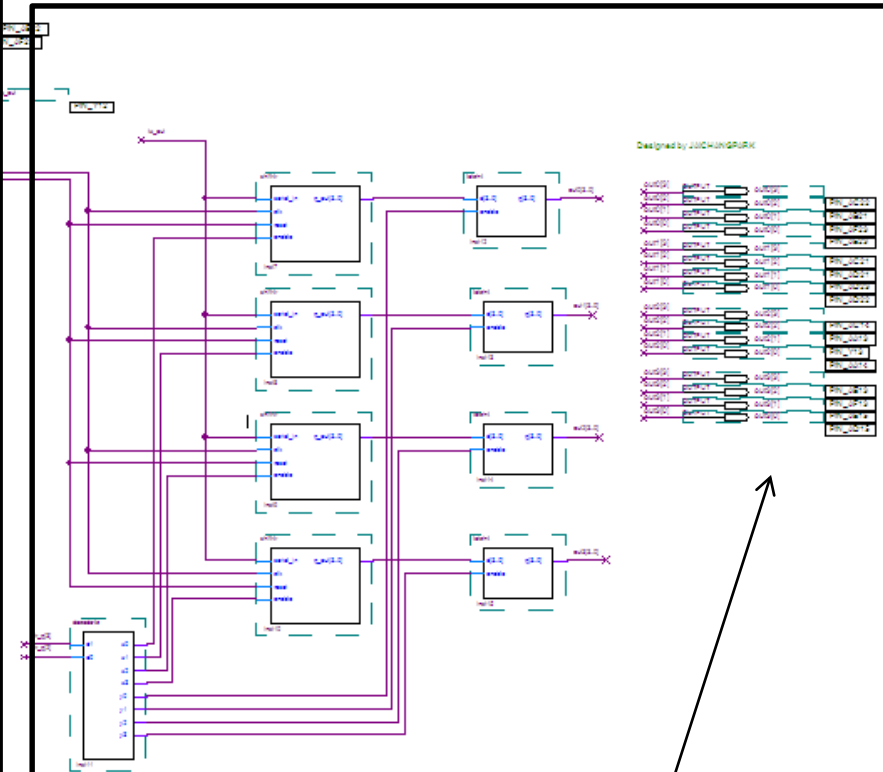

출력 신호 (발광다이오드)

# Time Division Multiplexing


- 결과 사진



회로 동작 상태 확인을 위한 led

# Time Division Multiplexing

## ■ 결과 사진

 

모든 입력 스위치를 0으로 설정했을 때


※입력부의 신호는 모두 0이기 때문에 수신부에서 수신한 발광 다이오드는 모두 발광하지 않고 꺼져있는 상태를 가진다.



# Time Division Multiplexing

## ■ 결과 사진


- 입력 Q3[3..0]
- 출력 out3[3..0]

 

입력 신호 스위치 q1, q3의 모든 스위치를 High state로 위치시켰을 때 설계한 시분할 멀티플렉서의 동작 확인 결과.  
송신부의 신호가 수신부의 신호로 정확하게 전달됨을 확인했다.

# Time Division Multiplexing

- 결과 사진

 

리셋 스위치 동작 시 모든 신호 Low state 전환으로 송신부 입력 스위치에 신호가 high state를 가져도 수신부의 신호는 전달 되지 못함

## Time Division Multiplexing

### ■ 결론

- 시분할 멀티플렉싱을 각 기능별 블록으로 제작해 전체 시스템 회로를 구성했다.
- 동작 검증은 1개의 DE2 단일 보드로 진행했으며 송신부의 입력은 스위치로 수신부의 수신 신호 확인은 led 발광다이오드로 동작을 확인했다.

**Thank you**

JAICHANG PARK